

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

B.Tech Degree S3 (R) (FT/WP) Examination November 2025 (2024 Scheme).

Course Code: PCECT303**Course Name: ANALOG CIRCUITS**

Max. Marks: 60

Duration: 2 hours 30 minutes

PART A*(Answer all questions. Each question carries 3 marks)*

CO Marks

- | | | | |
|---|--|---|-----|
| 1 | Explain why a fixed bias circuit is not widely used in amplifiers, despite its simplicity. | 2 | (3) |
| 2 | Design a low pass filter for a cutoff frequency of 5KHz. | 1 | (3) |
| 3 | Draw the frequency response of a CE amplifier. What is the significance of gain bandwidth product? | 2 | (3) |
| 4 | Explain the impact of the Miller effect on the frequency response of an amplifier. | 2 | (3) |
| 5 | Deduce the expression for closed loop gain A_f of a negative feedback amplifier. | 1 | (3) |
| 6 | Explain the criteria for sustained oscillations. | 1 | (3) |
| 7 | Why class AB power amplifiers are preferred over class B operations? | 2 | (3) |
| 8 | Define line regulation and load regulation, and discuss their importance in power supply design. | 1 | (3) |


PART B

(Answer any one full question from each module, each question carries 9 marks)

Module -1

9 a) What is thermal runaway? Explain the role of emitter resistance R_E in the potential divider biasing circuit. 1 (5)

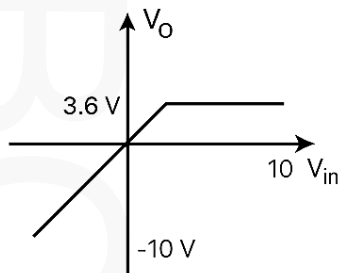b) Design a clipper circuit to obtain the following transfer characteristics. 1 (4)



10 a) Obtain the operating point set by the voltage divider bias circuit for an NPN transistor in common emitter configuration with $\beta = 50$ and $V_{BE} = 0.7$ V. Given $V_{CC} = 12$ V, $R_1 = 47$ k Ω , $R_2 = 10$ k Ω , $R_C = 2.2$ k Ω and $R_E = 680$ Ω . 2 (5)

b) Design a clamper circuit to clamp a 10Vpp sine wave so that positive peak is clamped at -3V. Draw the output waveform and transfer characteristics. Assume diode is ideal. 1 (4)

Module -2

11 a) Draw and explain the circuit of RC coupled amplifier and draw its frequency response curve. 2 (5)

b) Draw and explain the Common Source MOSFET amplifier. 2 (4)

12 a) Draw the small signal low frequency hybrid π model for common emitter configuration. Give the expression for voltage gain, input and output impedance. 2 (5)

- b) Three stages of individual RC coupled amplifier having mid-band gain of 80 with lower cut-off frequency of 100Hz and upper cut-off frequency of 300MHz are cascaded. Find the resultant gain and cut-off frequencies. 2 (4)

Module -3

- 13 a) With necessary diagram, explain the working of crystal oscillator. 2 (5)
- b) Explain voltage series feedback topology with neat block diagram. Derive the expression for net input and output impedance. 2 (4)
- 14 a) Draw the circuit of Wien bridge oscillator. Derive the expression for its frequency of oscillation. 1 (5)
- b) Explain the effect of negative feedback on gain, bandwidth, stability and distortion in feedback amplifiers. 2 (4)

Module -4

- 15 a) Explain the working of series voltage regulator. 1 (5)
- b) What is cross over distortion? How can it be overcome? 2 (4)
- 16 a) What is a Class B push-pull power amplifier? With necessary diagram Explain its working. 2 (5)
- b) With necessary diagram, explain the working of shunt voltage regulator. 1 (4)
